

Analog IC Design

**A Low-Power Low-Noise CMOS
Amplifier for Neural Recording
Applications**

Instructor: Prof. Abhishek Srivastava
Rohan Gupta – 2020112022

Introduction

The goal is to design a low-noise low-power bio signal amplifiers capable of amplifying signals in the millihertz-to-kilohertz range.

Fig. 1 shows the schematic of our bioamplifier design. Given in the paper.

 


Fig. 1. Schematic of neural amplifier.

Fig 1: Schematic of Neural Amplifier

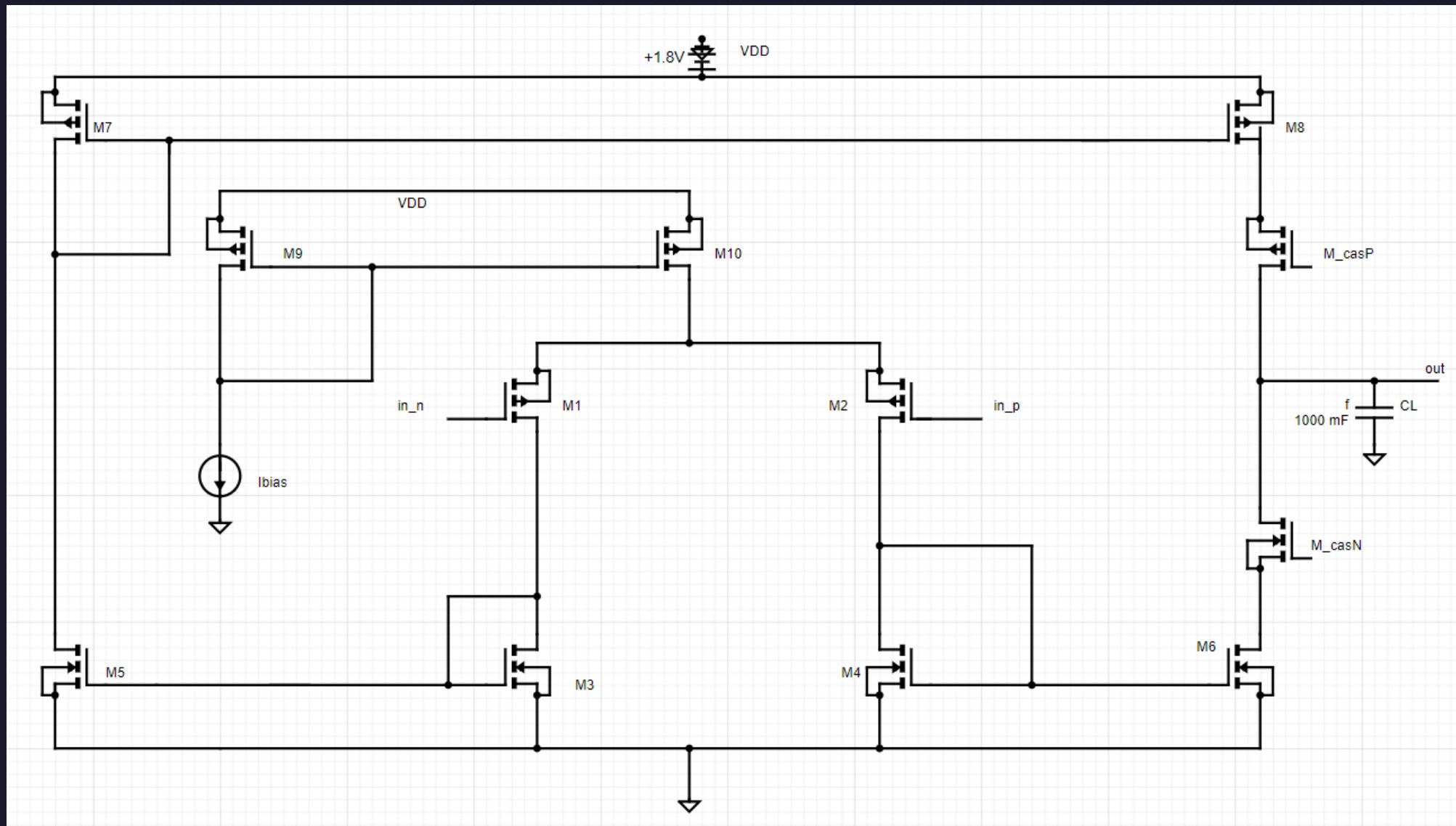


Fig 2: current-mirror OTA used in the bioamplifier.

Output transconductance Amplifier

- Fig. 4 shows a schematic of the current-mirror OTA used in the bioamplifier. The circuit topology is a standard design suitable for driving capacitive loads, the sizing of the transistors is critical for achieving low noise at low current levels.
- The bias current is set to 8 A, giving devices – drain currents of 4 A. At this current level, each transistor may operate in weak, moderate, or strong inversion depending on its ratio.
- Given Design Specification for the OTA:
 - DC gain $\geq 60\text{dB}$.
 - -3 dB bandwidth $\geq 10\text{ kHz}$.
 - Input referred noise $\leq 2\ \mu V_{rms}$.
 - CMRR $\geq 100\text{ dB}$.
 - Noise efficiency factor (NEF) ≤ 4
 - DC power consumption $\leq 30\ \mu\text{A}$
 - Supply voltage $\leq 1.8\text{ V}$



| Devices | ID(uA) | Inversion Coeffecient | Region of Operation |
|-------------|--------|-----------------------|-------------------------------|
| M1,M2 | 4 | <1 | Subthreshold(For greater gm1) |
| M3,M4,M5,M6 | 4 | >10 | Strong Inversion |
| M7,M8 | 4 | >10 | Strong Inversion |
| M9,M10 | 8 | >10 | Strong Inversion,Saturation |
| M_cascN | 4 | 1<IC<10 | Moderate Inversion |
| M_cascP | 4 | >10 | Saturarion |

DC gain = $(gm_1 * gm * r_o^2)/2$, gm_1 = Transconductance of M1, gm = Transconductance of Cascode Mosfets
 From Design Specifications,

1. For M1 ,M2 IC<1,

$$IC = \frac{Id}{Is} \rightarrow \frac{Id}{\frac{2\mu C_{ox} U_T^2}{\kappa} \cdot \frac{W}{L}} < 1 \quad \text{From the following we get } \left(\frac{W}{L}\right)_{1,2} > 444.44$$

2. Similarly for $M_{3-6} < 4.222$ $M_{7-8} < 3.4$

4. -3dB Bandwidth ≥ 10 KHZ (Dominant pole exists at -3db frequency)

$$\frac{1}{R_{out} * C_L} \geq 10 \text{ KHZ}$$

Assumed $C_L = 10$ f farad, $\Rightarrow As, R_{out} = (gm * r_o^2)/2$ and $r_o = 10^7$ ohm
 we get, $gm \leq 200 \mu S$

From gm, we get $\left(\frac{W}{L}\right)_{CasN} \leq 22.5$ and $\left(\frac{W}{L}\right)_{CasP} \leq 45$.

- Design Parameters from Hand calculation

| Devices | Type | W/L |
|-------------|-------|---------|
| M1,M2 | p18.7 | 80/0.18 |
| M3,M4,M5,M6 | n18.9 | 10/5 |
| M7,M8 | p18.9 | 5/10 |
| M9,M10 | p18.6 | 1.2/1.2 |
| M_cascN | n18.9 | 12/3.2 |
| M_cascP | p18.8 | 6.4/3.2 |

- Specification Achieved After Hand calculations:

| Specifications | Value |
|---------------------|--------------|
| Gain | 35.726628dB |
| Unity Gain Badwidth | 5.2966344MHz |
| Phase Margin | 55° |
| Gain Margin | 19.871138dB |



- Final Circuit with chosen MOSFET and sizing

| Devices | Type | W/L | Hand Calculated |
|-------------|-------|---------|-----------------|
| M1,M2 | p18.7 | 80/0.18 | 80/0.18 |
| M3,M4,M5,M6 | n18.9 | 27/3 | 10/5 |
| M7,M8 | p18.9 | 2/9 | 5/10 |
| M9,M10 | p18.6 | 1.2/1.2 | 1.2/1.2 |
| M_cascN | n18.9 | 40/5 | 12/3.2 |
| M_cascP | p18.8 | 90/1 | 6.4/3.2 |
| CL | 0.5pF | 1f | |


- Specification Achieved After Final design:

| Specifications | Value |
|---------------------|--------------|
| Gain | 62.117163dB |
| Unity Gain Badwidth | 5.4450265MHz |
| Slew Rate | 5.1 MV/s |
| Phase Margin | 42.80548° |
| Gain Margin | 5.588399dB |

Pseudo PMOS Resistor

- The pseudo resistor is capable of resisting large DC offsets and provide stability when used in feedback
 
```
.dc v1 -1 1 0.01  
.lib 'ts18sl_scl.lib' tt_18dll
```




```

.lib 'ts18sl_scl.lib' tt_18dll
.param L = 1u W=10u n = 1 LAMBDA = 0.09u
.lib 'ts18sl_scl.lib' tt_18
;noise V(out) v1 dec 1000 1 1G
.ac dec 1000 1 10G
.op
;dc V3 0 3 0.001

```


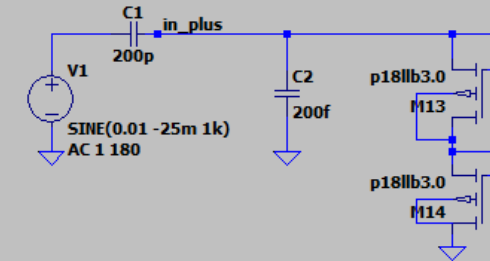
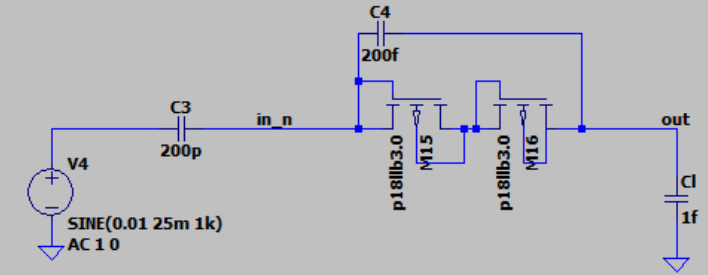
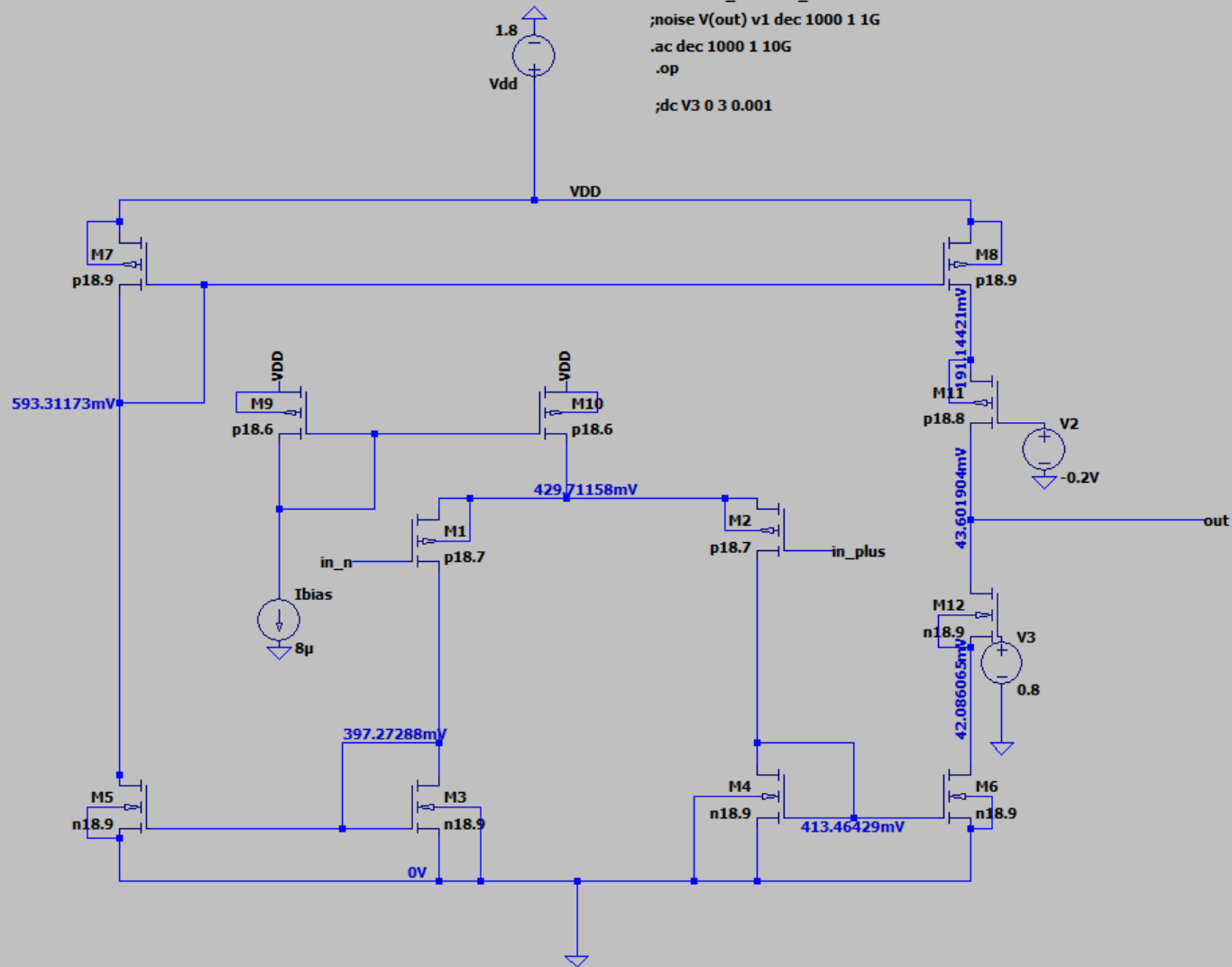


Fig: Neural Amplifier Schematic

Neural Amplifier

| Specifications | Value |
|---------------------|-------------|
| Gain | 1.3262585dB |
| Unity Gain Badwidth | 2.837919MHz |

 

Final Design and Results:

| Performace | OTA |
|---------------------|--------------|
| Gain | 62.117163dB |
| Unity Gain Badwidth | 5.4450265MHz |
| Slew Rate | 5.1 MV/s |
| Phase Margin | 42.80548° |
| Gain Margin | 5.588399dB |
| ICMR | 1.22 V |
| CMRR | 103.699053dB |
| PSRR | 60.19 dB |
| RMS Noise | 401.77μV/√Hz |
| Power | 43.452uW |